

ADC Section 3

2025年11月11日 星期二

09:35

ADC s.s.:

7 November, 2025

Lab, Charles Wu.

Reference, ADC section 3

Aim: Test for 1st and 2nd order filters.

Procedure:

• Before the lab.

I am allocated to build a: high-pass filter with 7300Hz corner frequency with $Z=1$

For high-pass, $H = \frac{Z}{R + Z} = \frac{1}{R + 1 + LC\omega^2}$

$\therefore \omega_c = \frac{1}{\sqrt{LC}} = \sqrt{\frac{1}{LC}} = \frac{1}{\sqrt{LC}}$

$\therefore \sqrt{\frac{1}{LC}} = 2\pi \times 7300 \text{ rad/s}$

$Z = \frac{R}{1 + LC\omega^2} = \frac{R}{1 + LC(2\pi \times 7300)^2} = \frac{R}{1 + LC(2\pi \times 7300)^2}$

$\therefore \frac{R}{1 + LC(2\pi \times 7300)^2} = 1 \text{ } \Omega$

$\therefore$ I choose 1mH inductor,

$\sqrt{\frac{1}{LC}} = 2\pi \times 7300$

$C = \frac{1}{(2\pi \times 7300)^2 \times 10^{-3}} \text{ F} \approx 470 \text{ nF}$

$\frac{R}{1 + LC(2\pi \times 7300)^2} = 1$

$\therefore R = 91.74 \Omega \approx 91 \Omega$

$L = 1 \text{ mH}$


$C = 470 \text{ nF}$

$R = 91 \Omega$

• First-order filter.


For each group of high-pass and low-pass filter, we measure impedance of capacitor across different frequency, to find out overall trend of $|Z|$ across frequency, and find the corner frequency.

For a low-pass filter.

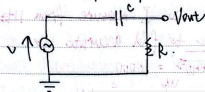

Resistance/Ohm	Capacitance/uF	Frequency/Hz	DeltaT/s	Vout/V	Vin/V	Arg(T(f))	T(f) /V
1000	1	1	0.00242	1.72	1.73	0.015205308	0.994218653
1000	1	10	0.00104	1.79	1.81	0.055345127	0.988950276
1000	1	100	0.00083664	1.45	1.72	0.525676416	0.843023256
1000	1	320	0.00083232	0.77718	1.66	1.673478654	0.468180723
1000	1	1000	0.0002172	0.29232	1.66	1.364707849	0.176096386
1000	1	3200	0.0000739	0.09492	1.65	1.485847661	0.057527273
1000	1	10000	0.00002436	0.03099	1.64	1.530583941	0.018896341
1000	1	50000	0.00000492	0.00573	1.5	1.545663586	0.00382


For a high-pass filter.

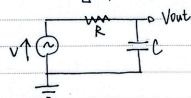


Resistance/Ohm	Capacitance/uF	Frequency/Hz	DeltaT/s	Vout/V	Vin/V	Arg(T(f))	T(f) /V
1000	1	1	0.22772	0.01133	1.73	1.430806958	0.006549133
1000	1	10	0.02333	0.11102	1.81	1.465867132	0.061337017
1000	1	100	0.00165	0.88272	1.71	1.036725576	0.516210526
1000	1	320	0.000244	1.46	1.66	0.490591109	0.879518072
1000	1	1000	0.0000284	1.62	1.64	0.178442463	0.987804878
1000	1	3200	0.0000028	1.64	1.65	0.05629734	0.993939394
1000	1	10000	0.00000038	1.65	1.66	0.023876104	0.993975904
1000	1	50000	0.00000001	1.51	1.51	0.003141593	1

For low-pass:

$|T(f)|/V$ vs. Frequency/Hz


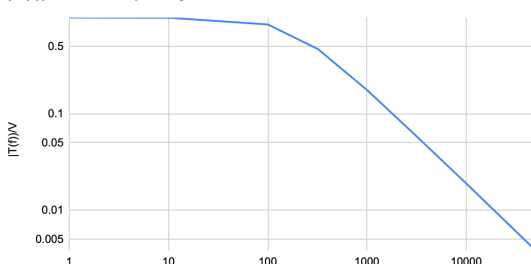


$\text{Arg}(T(f))$ vs. Frequency/Hz

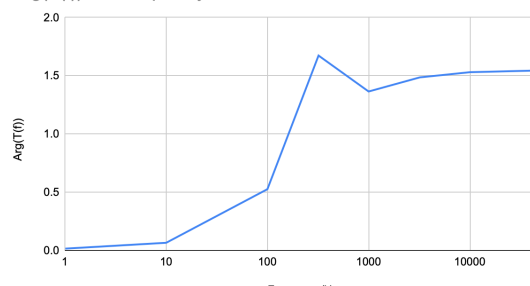



For high-pass:

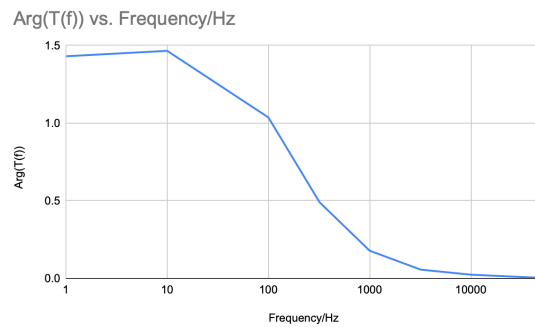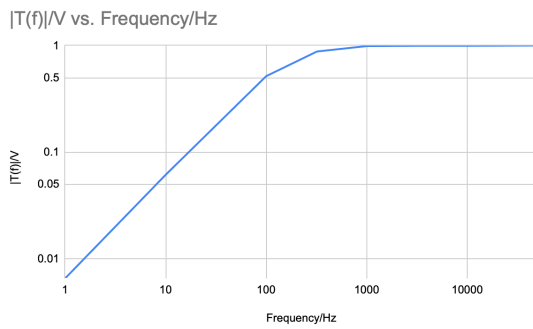

They work well and align with the low-pass and high-pass filters' functions.

• Resonant networks.
Using some method of CH1, CH2, to measure impedances of series and parallel LC network, and find resonant frequency.

Note: At first, I didn't see that we have to predict ω_0 , which is $\omega L = \frac{1}{\omega C} = 0$
 $\omega_0 = \frac{1}{\sqrt{LC}}$, so I measure from 1 Hz to 10 kHz, which makes it impossible to find accurate ω_0 .
then I do $\omega_0 = \sqrt{\frac{1}{LC}} = 6000$
 $\therefore f = \frac{\omega_0}{2\pi} = 1591.5 \text{ Hz}$,
so measure from 1000 ~ 2000 Hz:

Series network:

Resistance/Ohm	Vz/V	VR/V	impedance/Ohm	Frequency/Hz
1000	1.72	1.11	1549.5495	1000
1000	1.71	1.27	1346.6567	1200
1000	1.71	1.36	1257.3529	1400
1000	1.7	1.38	1231.8641	1500
1000	1.66	1.35	1229.6296	1600
1000	1.66	1.34	1238.806	1620
1000	1.66	1.35	1229.6296	1640
1000	1.66	1.35	1229.6296	1660
1000	1.66	1.34	1238.806	1700
1000	1.71	1.37	1248.1752	1800
1000	1.72	1.32	1363.9303	2000
1000	1.72	1.25	1376	2200

Parallel network:

Resistance/Ohm	Vz/V	VR/V	impedance/Ohm	Frequency/Hz
5000	1.72	1.54	5584.415584	1000
5000	1.72	1.42	6056.338028	1200
5000	1.72	1.19	7228.890756	1400
5000	1.72	1.02	8431.972549	1500
5000	1.72	0.90228	9531.409319	1600
5000	1.72	0.89855	9570.97546	1620
5000	1.72	0.90422	9510.697122	1640
5000	1.72	0.93232	9224.300669	1660
5000	1.72	1.12	7678.571429	1800
5000	1.72	1.4	6142.857143	2000
5000	1.72	1.54	5584.415584	2200


Wrong version:

Resistance/Ohm	Vz/V	VR/V	impedance/Ohm	Frequency/Hz
1000	1.39	0.98022	1418.049009	1
10000	1.8	0.11265	159786.9507	10
10000	1.74	0.34354	50649.12383	32
10000	1.46	0.89991	16223.84461	100
10000	0.18376	1.67	1100.359281	1000
10000	0.88317	1.45	6090.827586	10000
10000	1.51	0.68687	21983.7815	32000
10000	1.53	0.37534	40763.04151	50000




Resistance/Ohm	Vz/V	VR/V	impedance/Ohm	Frequency/Hz
1000	0.29404	1.37	214.6277372	1
1000	0.30505	1.42	214.6239437	3.2
1000	0.30794	1.43	215.3426573	10
1000	0.30411	1.41	215.6808511	32
1000	0.30854	1.37	225.2116788	100
1000	0.40783	1.33	306.6390977	320
1000	0.99412	0.94008	1057.484469	1000
1000	0.29095	1.63	178.4969325	10000

Series network: Can observe that the lowest impedance, which is at the resonant frequency is at near 1600Hz. The graph aligns with the data.

impedance/Ohm vs. Frequency/Hz

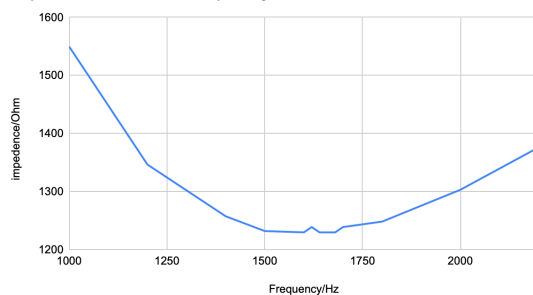

impedance/Ohm vs. Frequency/Hz
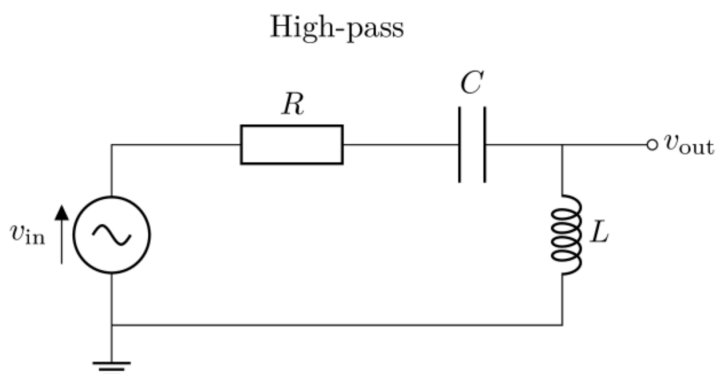  
|T(f)|/V vs. Frequency/Hz