

## Section 1: Current Mirrors

2026年2月17日 星期二 14:03

### Introduction

An operational amplifier has several ideal parameters, including:

- Very high differential gain
- Very low common-mode gain
- Very high input impedance
- Very low output impedance

The aim of this experiment is to explore how BJT building blocks can achieve these properties and be combined to make a working opamp.

### Background

We can build 3 different stages to achieve requirements for an ideal op-amp.

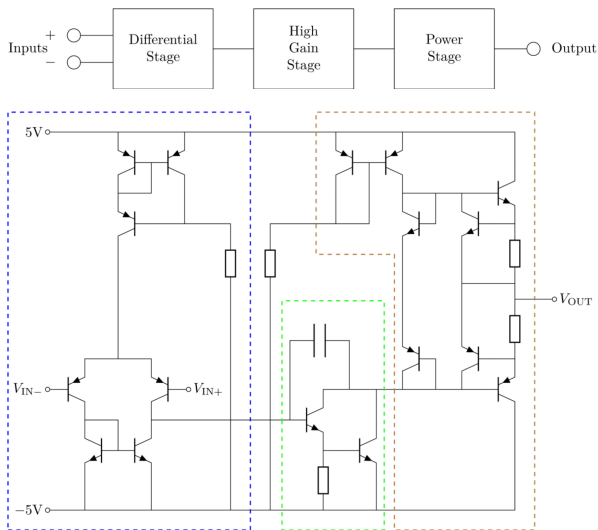


Fig1. 3 Stages in an op-amp.

The behaviour of the BJTs is defined by the usual expressions:

$$I_C = I_S e^{\frac{V_{BE}}{V_T}} \left( 1 + \frac{V_{CE}}{V_A} \right)$$

For  $V_A \gg V_{CE}$ , this is approximated as:


$$I_C = I_S e^{\frac{V_{BE}}{V_T}}$$

We will also use the small signal output impedance:

$$r_0 = \frac{V_A}{I_C}$$

### Current Mirror and Current Source

The current mirror is a widely used building block that acts as a current buffer. The current flowing in the input branch of the circuit is mirrored so that the same current also flows in the output branch. An ideal current mirror has an infinite output impedance since it acts like a current source. It can be built with PNP transistors to make a source of positive current, and NPN transistors to make a current sink.

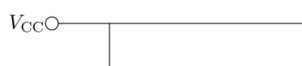


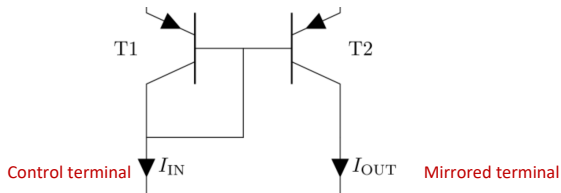


Fig2. Simple Current Mirror

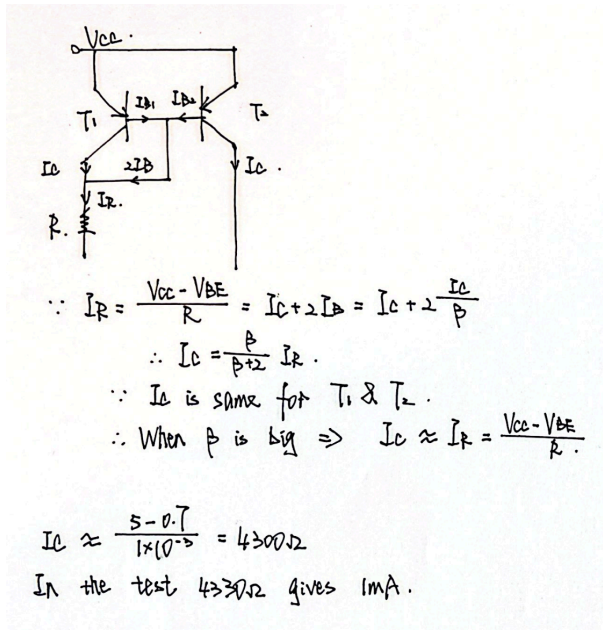

Simulate the current mirror with  $V_C = -15V$  using this circuit:

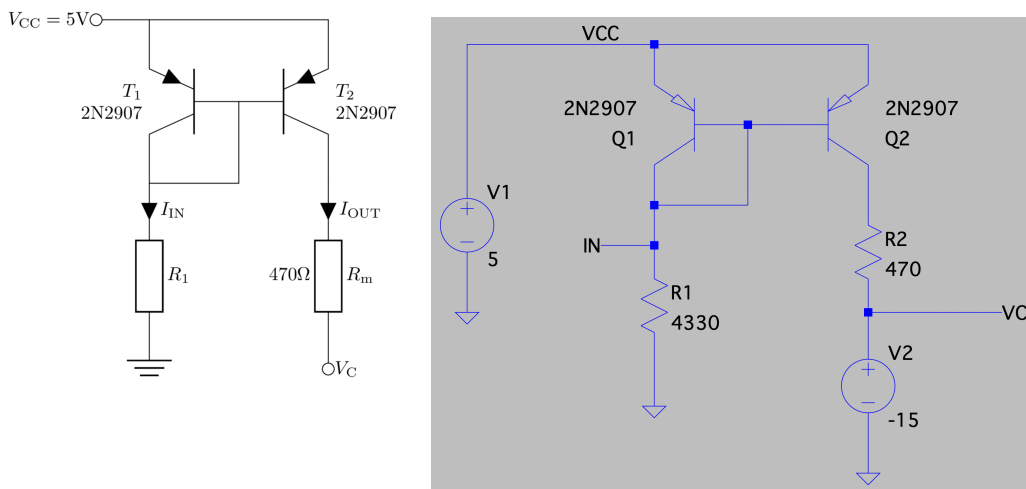


Fig3. Simulated Circuit

In this case T1 is diode-connected.

Choose a value of  $R_1$  so that  $I_{IN} = 1 \text{ mA}$ .

Draft2.log

| Node     | Value        | Unit           |
|----------|--------------|----------------|
| V(in)    | 4.34462      | voltage        |
| V(vcc)   | 5            | voltage        |
| V(in001) | -14.4595     | voltage        |
| V(vc)    | -15          | voltage        |
| Ic(01)   | -0.000995392 | device_current |
| Ib(01)   | -3.59472e-06 | device_current |
| Ie(01)   | 0.000999386  | device_current |
| Ic(02)   | -0.00115     | device_current |
| Ib(02)   | -3.58956e-06 | device_current |
| Ie(02)   | 0.00115399   | device_current |
| I(R1)    | 0.00100338   | device_current |
| I(R2)    | 0.00115      | device_current |
| I(V2)    | -0.00115     | device_current |
| I(V1)    | 0.00215338   | device_current |

Total elapsed time: 0.019 seconds.

Fig4. 1mA

Run a DC analysis to find  $I_{IN}$  and  $I_{OUT}$ . What is the *current transfer ratio* between input and output?

So our  $I_{IN}$  &  $I_{OUT}$  is:

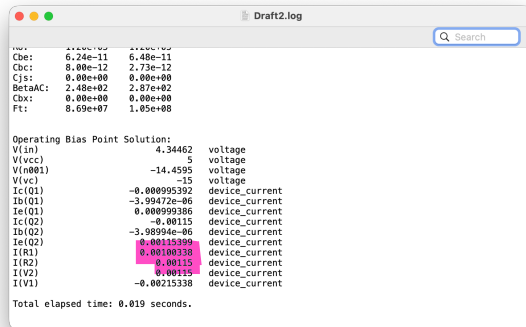


Fig5.  $I_{OUT}$  &  $I_{IN}$  of Current Mirror

$$\text{Ratio} = I_{OUT}/I_{IN} = 0.00115/0.00100338 = 1.14612609$$

The current mirror can be compared to an ideal current source by finding its output resistance  $R_{OUT}$ . Find this by varying  $R_{OUT}$  between -15V and -5V. You can use the 'DC Sweep' simulation mode, which allows you to step the value of  $V_C$  and record the output current for each step.

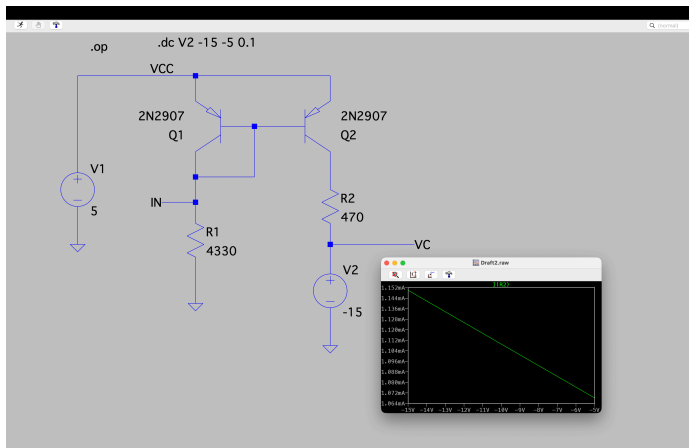




Fig6. DC Sweep

$$R_{OUT} = \frac{\Delta V_C}{\Delta I_{OUT}}$$

We get 2 points:  
 (-13.91V, 1.14102mA)  
 (-5.69V, 1.07367mA)

$$R_{OUT} = 122049.0\text{ohm}$$

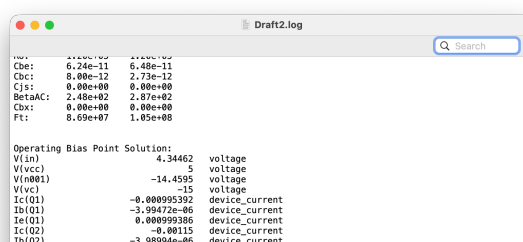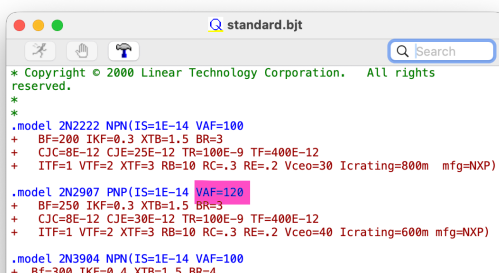Find the output resistance of the current mirror. Does it match the predicted output resistance  $r_o = V_A/I_C$ ?



```

+ CJC=4E-12 CJE=8E-12 RB=20 RC=0.1 RE=0.1
+ TR=250E-9 TF=350E-12 ITF=1 VTF=2 XTF=3 Vceo=40 Icrating=200m
mfg=NXP)

.model 2N3906 PNP(IS=1E-14 VAF=100
+ BF=200 IKF=0.4 XTB=1.5 BR=4
+ CJC=4.5E-12 CJE=10E-12 RB=20 RC=0.1 RE=0.1
+ TR=250E-9 TF=350E-12 ITF=1 VTF=2 XTF=3 Vceo=40 Icrating=200m
mfg=NXP)

.model FZT849 NPN(IS=5.8591E-13 NF=0.9919 BF=230 IKF=18 VAF=90
+ CJC=3.0637E-12 CJE=1.44E-12 RB=0.0000 RD=100 Icrating=200m
mfg=ON)

```

```

Ie(O2)      0.00115399 device_current
I(R1)        0.00100338 device_current
I(R2)        0.00115 device_current
I(V2)        0.00115 device_current
I(V1)       -0.00215338 device_current

Total elapsed time: 0.019 seconds.

```

Fig6. Characteristic of 2N2907 in Simulating Tool

So theoretical  $r_0 = V_A/I_C = 120/0.00115 = 104,347.82609\text{ohm}$ .  
Error = 14.5%, match.

## Wilson Current Mirror

The simple current mirror has a few sources of inaccuracy:

- $I_C$  for the two transistors is only equal if the transistors are identical. In simulation this is true, but in practice transistors will have slightly different  $I_C$  for the same  $V_{BE}$
- $I_{IN}$  includes the  $I_B$  of  $T_2$  and, since  $\beta$  is finite, this causes a difference between the currents
- BJTs have a finite output resistance and  $I_{OUT}$  will depend on  $V_{CE}$  of  $T_2$

A much higher quality current-mirror can be obtained by the addition of just a single transistor, connected between the input and the output of the simple current-mirror. The modified circuit is shown below — it is known as the Wilson current mirror after its inventor.


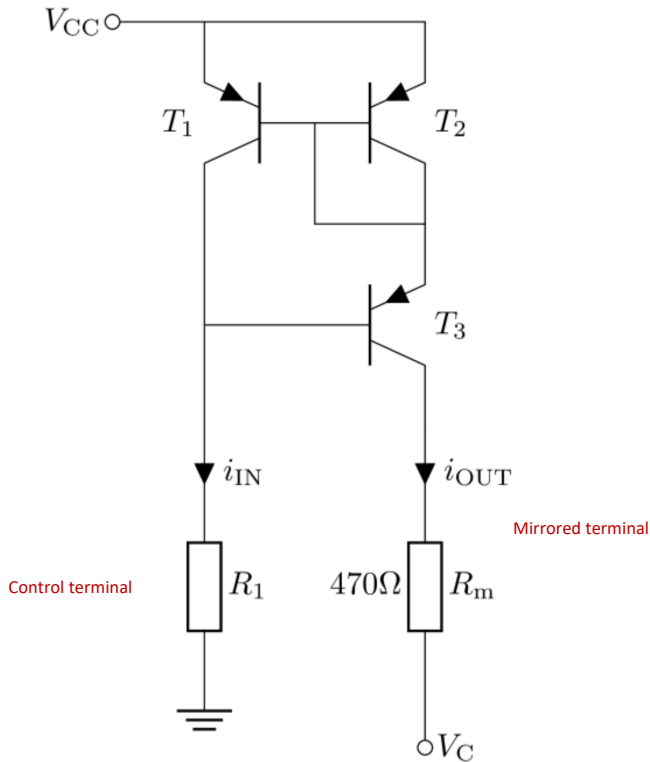


Fig7. Wilson Current Mirror

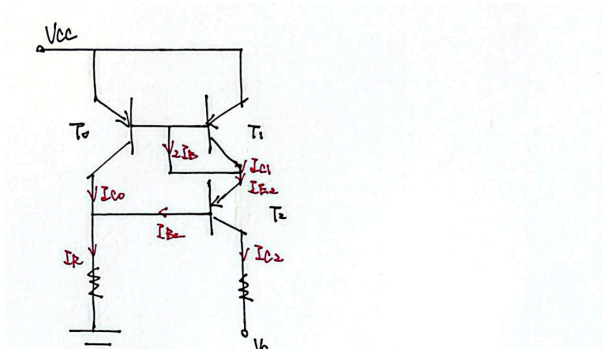The extra transistor,  $T_3$ , now accounts for most of the voltage drop between  $V_{CC}$  and the output. That means  $T_1$  and  $T_2$  have a similar  $V_{BE}$  and therefore  $I_C$  of the two transistors is closer.  $T_3$  also cancels out the effect of the base current in the output and reduces the error due to finite  $\beta$ .



$$\begin{aligned}
 \therefore I_{E2} &= I_C + 2I_B = \frac{\beta+2}{\beta} I_C \\
 I_C &= \frac{\beta}{\beta+2} I_{E2} = \frac{\beta}{\beta+2} \cdot \frac{1+\beta}{\beta} I_{C2} = \frac{\beta+1}{\beta+2} I_{C2} \\
 I_R &= I_{E2} + I_C = \frac{I_{C2}}{\beta} + \frac{\beta+1}{\beta+2} I_{C2} = \frac{(\beta+1)(\beta+2)}{\beta^2+2\beta} I_{C2} \\
 I_{C2} &= \left(1 - \frac{2}{\beta^2+2\beta+2}\right) I_R \approx I_R
 \end{aligned}$$

So now difference in 2 currents is a second-order difference in beta, which will be significantly reduced.

However, there is still an error because:

1. It is still dependent of beta, and beta is not infinite.
2. BJTs still have Early-Voltage resistance, so they will share the current.

Choose the value of  $R_1$  so that  $I_{IN} = 1$  mA again. Note that the voltage of the input node is now  $V_{CC} - 2V_{BE}$ .

Repeat the characterization of the current mirror and look for an improvement in the current transfer ratio and output impedance.

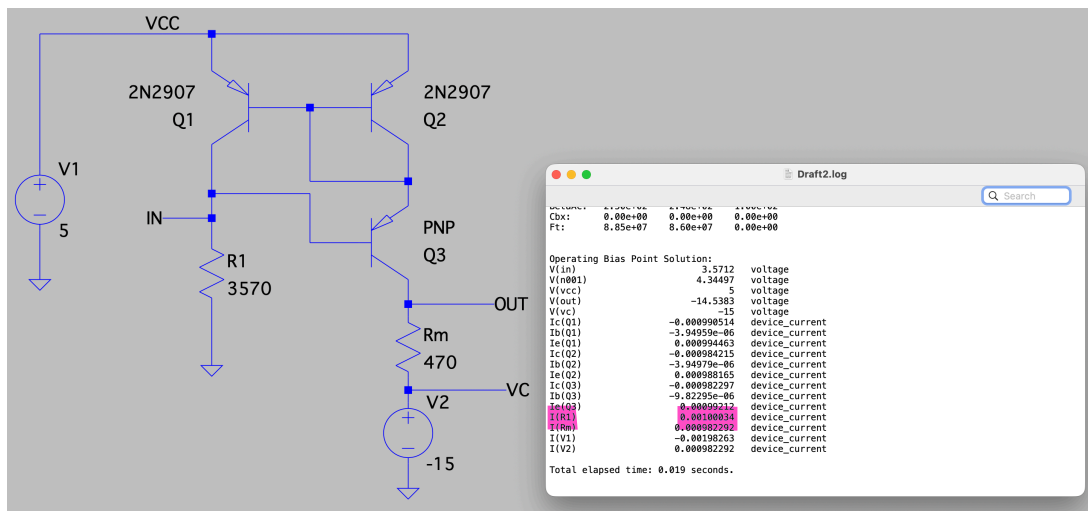


Fig8. Check For 1mA

Ratio =  $I_{OUT}/I_{IN} = 0.000982292/0.00100034 = 0.981958134$ .  
So better than before.

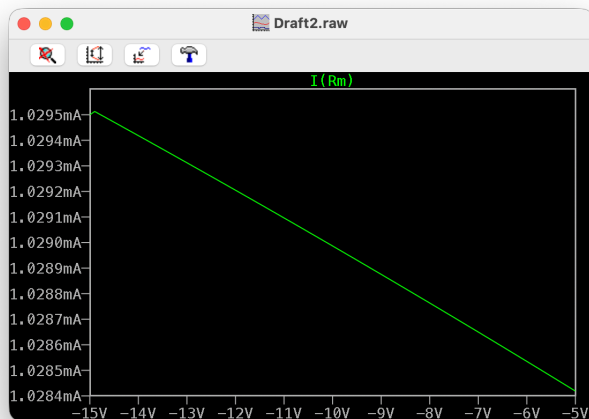


Fig9. Check for Output Resistance

(-14.26V, 1.029443mA)  
(-5.68V, 1.028496mA)

$R_{OUT} = 9060190.0\Omega$ , which is reasonable.