

DECA Section 1

2025年11月11日 星期二 08:27

Digital Electronics & Computer Architecture Lab - S1.
14 October, 2025.
Lab, Charles Wu.

Reference: DECA Section 1.

Aim. Learn how to use ISSIE, design multiplexers & simple ALU.


Procedure.

- Building a simple AND gate and simulate it works by truth table.

what expect to get:

A	B	Y
0	0	0
0	1	0
1	0	0
1	1	1

$$Y = A \cdot B$$

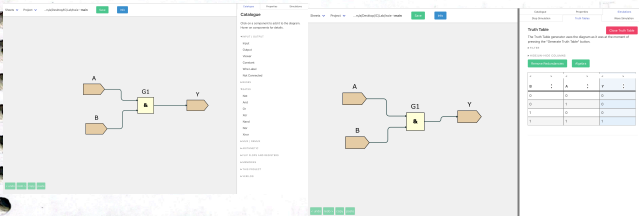


Which is true

- Building a 2-input multiplexer using AND, OR, and inverter.
A multiplexer controls which input to use when there are several inputs and sends the right one to output.

It has boolean expression: $Y = A \cdot \bar{S} + B \cdot S$ (2-input)

Expect:

S	Y
0	A
1	B

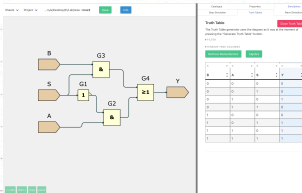

- Trying hierarchical design and create a 4-input multiplexer.


Equation: $Y = A\bar{S}_0\bar{S}_1 + BS_0\bar{S}_1 + C\bar{S}_0S_1 + DS_0S_1$

Expect:

S0	S1	Y
0	0	A
0	1	B
1	0	C
1	1	D


A	B	C	D	S0	S1	Y
A	B	C	D	0	0	A
A	B	C	D	0	1	B
A	B	C	D	1	0	C
A	B	C	D	1	1	D

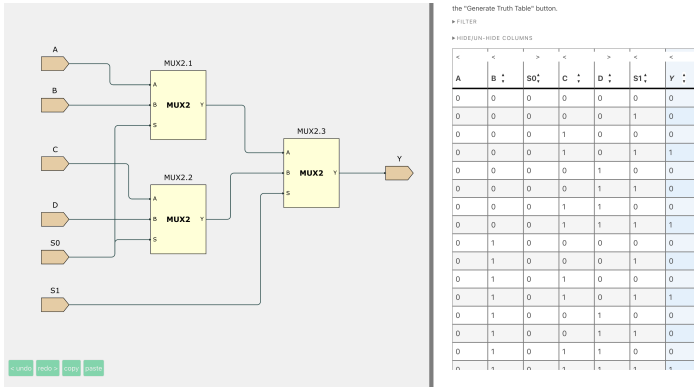- This can be done by using 2-input (MUX2) as sub-sheet.
A and B can go through MUX2; C and D go through another MUX2;
then the results of AB and CD goes through a third MUX2 to finally locate an accurate one.



For SELECT, one select controls up to $2^1 = 2$ inputs
 $2^2 = 4$
 $2^3 = 8$

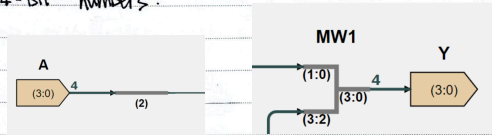- Learning to use 'MergeWires' & 'BusSelect' for entering 4-bit numbers.




One technique is that we can only test AB to check for MUX 2×4 , as MUX 2 functions well.

Expect:

A	B	S	Y
000	110	0	000
001	110	1	110
100	011	0	100
101	011	1	011

which is correct.

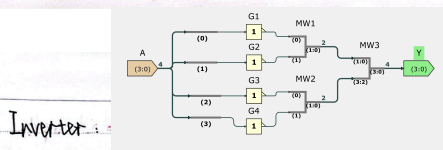- Challenge: Building a simple ALU for 2 inputs of 4-bits, including: NOT A; A OR B; A AND B; A XOR B. Just merge what we've learned, build 4 operations in sub-sheet first, then use them in the 'main', use a MUX to select needed data.




Inverter:

2×4 XOR

2×4 AND

2×4 OR

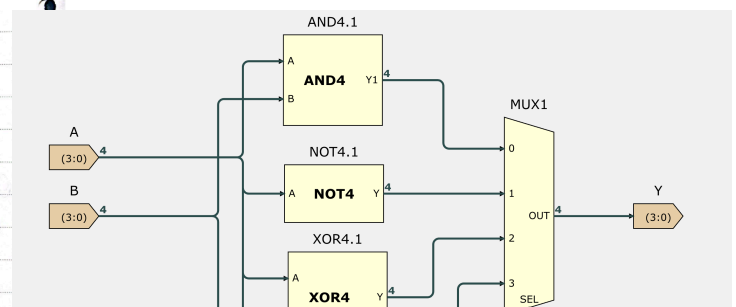

After merging:

Do a random test, I use.

A	B	S ₀	S ₁	Y
1010	0110	0	0	0101
1010	0110	0	1	1110
1010	0110	1	0	0010
1010	0110	1	1	1100

which gives correct results of NOT A, A1B, A2B, A3B in order.

Final.

