

Section 1

2025年12月9日 星期二 13:25

Digital Electronics & Computer Architecture Lab. S1.
1st December 2025
Lab, Charles Wu.

Reference: DECA Parts, section 1.

Aim: Learn about memory, build a ROM, which stores a message ≤ 15 words inside; and build a message writer with trigger as challenge.

Procedure.

• Before the lab:

Memory allows storage of large blocks of data. One word of data can be accessed by computer at once in the memory as following:

 


Fig1.1

Before the lab, we need to know about ASCII symbols, and prepare a personalised text message in hexadecimal format.

Mine is: S H A N G H A I.

which is: 0x53 0x48 0x41 0x45 0x47 0x48 0x41 0x49.

which includes 8 characters in total.

• Initialising ROM

Contents in ROM must be defined when it's created and cannot change at runtime.

We use a synchronous ROM, which requires a rising clock edge to update output to do experiment. I enter the text message "SHANGHAI" as following:

 


Fig1.2

• Simulating ROM.

After adding address A & output D ports, where the A is 4 bits to select 16 outputs; D is 8 bits same as ASCII symbol of letters. $\therefore$ ROM is clocked, $\therefore$ it will only update output when it receives a rising clock.

Set A = 2; 5; 7

Expect to get D = x41; x48; x49 when clock rises, and the result is as expected:

 


Fig1.3

hex dec bin

Inputs

A (4 bits) 2

Outputs & Viewers

D (8 bits) x41

Stateful components

hex dec bin

Inputs

A (4 bits) 5

Outputs & Viewers

D (8 bits) x48

Stateful components

RAM: ROM1

View

hex dec bin

Inputs

A (4 bits) 7

Outputs & Viewers

D (8 bits) x49

Stateful components

Fig1.4, 1.5, 1.6

Challenge: Message Writer

We need to connect a counter (in part 1, section 3) to ROM, so that it will output each character in message sequentially. It will automatically cycle through message with 1-tick delay, as the ROM is synchronous.

After importing my counter, I made the following changes:

- ① Set $C_1 = \text{bool}$, so that counter + bool each tick
- ② Set $C_2 = 0$, which is addition (0 for add; 1 for subtract)
- ③ Set bus-compare to $\text{bool} (=1)$, as there're 8 bits in my message, so counter will cycle from $0000 \sim 1011$.

Note: I search online and realise bus-compare are XOR gates, it will output 0 if $A \neq B$, 1 if $A = B$, which inputs back to MUX to choose cycle or +1.

Also, another notice is that the default input for a no-input component is 0, so my counter will start at 0.

My counter is like:

 


Fig1.7

where D here is a starting point after 1st row.


If set $D = n$, ROM will go: $0-1-2-3-4-5-6-7-n-(n+1)\dots-1-N$ because MUX will select n to be next; $-(n+1)\dots-1-N\dots$

if output = 7.

Example $n=5$: S-H-A-N-G-H-A-I-H-A-I-H-A-I...

If just wants SHANAHAI cycle: set $D=n=0$.

As expected:

 

Challenge II: adding a trigger

In this task we need to add a trigger: if trigger = 1, ROM will run as normal. As long as trigger = 0, ROM will run to end of this cycle and stop. If trigger = 0 and ROM is at 0, it will never run which indicates as table:

Counter	Condition	Next value
$Q=0$	$T=0$	0
$Q=0$	$T=1$	$Q+1$
$0 < Q < N-1$	Always	$Q+1$
$Q = N-1$	Always	0

We now need to add additional MUX and logics to make this design.

My idea is as following: I add a built-in trigger into counter to control selection of 0 or +1 in counter. And trigger is controlled by logics in big circuit.

 


Fig1.13

 


Fig1.14 For counter2

① I consider all conditions that out = 0.

hex dec bin

Inputs

A (4 bits)

0

Outputs & Viewers

D (8 bits)

x47

Stateful components

RAM: ROM1

hex dec bin

Inputs

A (4 bits)

0

Outputs & Viewers

D (8 bits)

x4E

Stateful components

RAM: ROM1

hex dec bin

Inputs

A (4 bits)

0

Outputs & Viewers

D (8 bits)

x47

Stateful components

RAM: ROM1

hex dec bin

Inputs

A (4 bits)

0

Outputs & Viewers

D (8 bits)

x47

Stateful components

RAM: ROM1

hex dec bin

Inputs

A (4 bits)

0

Outputs & Viewers

D (8 bits)

x47

Stateful components

RAM: ROM1

hex dec bin

Inputs

A (4 bits)

0

Outputs & Viewers

D (8 bits)

x47

Stateful components

RAM: ROM1

The first is $in=0$ & trigger = 0
 The second is $in=N-1$, no matter trigger's state.
 ③. For $in=0$ & trigger = 0, I add a bus-compare to compare in , if $in=0$. Compare inputs 1 into MUX, and MUX outputs trigger value into trigger2. if trigger = 1, $\therefore$ there's an OR gate in counter, so (A or D) always give A, counter runs as normal and will not be affected. If trigger = 0, then the OR gate (A or 1) will always give D, which means it stays at D.
 ④. For $in \neq 0$, then in big circuit, bus-compare always inputs 0 into MUX and trigger2 is fixed at 1, like former case, counter runs as normal. *like before.*
Note: we set D=0, so ROM stays at 0 for $in=0$ & trigger=0.
 Test and it's like expected.

 


Fig1.15 Remains at 0 when trigger=0

 


Fig1.16 Run when trigger=1

 


Fig1.17, 1.18 Continue to end when trigger=0 again; stop at 0