

Section 6

2026年1月28日 星期三


16:19

6 CMP and AND instructions

Task 6. Using the material from Lecture 3 and Figure 8, review the behaviour of the CMP instruction in detail and compare it with the other ALU instructions that use ADDSUB.


1. **CMP vs SUB.** The instruction **CMP** performs a subtraction internally, but its purpose is to update flags rather than to write a data result.

 i. Identify which piece of hardware is responsible for the difference in behaviour between SUB and CMP. In particular, discuss the significance of the signal DPDECODE.WEN1



Difference is in DPDECODE, when CMP chosen, WEN1 will be 0, so that Reg File won't write in anything. When CMP not chosen, WEN1 will be 1 (default value) so that data is written to Reg File.

 ii. Inspect the logic in the ddecode sheet that drives DPDECODE.WEN1. You may assume that, for this question, JSR = 0 and LDR = 0.



(15) is always 0, so it enters G1 and becomes 1. When CMP chosen, It enters G3 = 0. In G4, 0&1 gives 0, and in G2 and G10, output is still 0.


When CMP unchosen, output of G3 = 1, so in G4, 1&1 gives 1. And the final output Is 1. So Reg File begins to write in numbers.

iii. Write a truth table that shows the value of WEN1 for each of the eight ALU instructions shown in Figure 7. Explain what this table shows about when the ALU result is written back to the register file and when it is not.

ALU instruction	WEN1	Write or not
MOV	1	Yes
ADD	1	Yes
SUB	1	Yes
ADC	1	Yes
SBC	1	Yes
AND	1	Yes
CMP	0	No
SHIFT	1	Yes

2. AND instruction. Look at the multiplexers (MUX2) in the alu sheet and the encoding of the AND instruction in the instruction set.

 i. Identify the hardware that implements the AND instruction: which input signals feed the logic block, and through which mux selection does the ALU choose the AND result?



2 inputs, which are RA, and a chosen between immediate and RB enter the AND logic. And ALU chooses AND at 5 in MUX2.

1 2 3 1040 1

I do 2 tests. In the test, RA=b1111,1111,1111,1111;
RB=b0000,0000,1111,1111;
OP2SEL = 0 so it selects RB;
ALUOPC = 0101 and 1101 separately.

When ALUOPC = 0101, it is AND Gate and OUT
is expected to be b0000,0000,1111,1111

hexdecbin

bin

Inputs

RA (16 bits)

b1111,1111,1111,1111

ALUOPC (4 bits)

b0101

SHIFTOPC (2 bits)

b00

OP2SEL

0

SCNT (4 bits)

b0000

FLAGCIN

0

RB (16 bits)

b0000,0000,1111,1111

IMM (16 bits)

b0000,0000,0000,0000

Outputs & Viewers

FLAGC

1

FLAGV

0

OUT (16 bits)

b0000,0000,1111,1111

When ALUOPC = 1101, it is OR Gate and OUT
is expected to be b1111,1111,1111,1111

hexdecbin

bin

Inputs

RA (16 bits)

b1111,1111,1111,1111

ALUOPC (4 bits)

b1101

SHIFTOPC (2 bits)

b00

OP2SEL

0

SCNT (4 bits)

b0000

FLAGCIN

0

RB (16 bits)

b0000,0000,1111,1111

IMM (16 bits)

b0000,0000,0000,0000

Outputs & Viewers

Outputs & viewers

FLAGC

1

FLAGV

0

OUT (16 bits)

b1111,1111,1111,1111

As expected.