

ADC Section 1

2025年11月11日 星期二

08:53

Analysis & Design of Circuits Lab. Si

24 October, 2025

Lab, Charles Wu.

Reference: ADC section 1.

Aim: Measure impedance of resistors and parasitic impedance of signal generator.


Procedure.

• Measuring impedance of simple resistor.



∵ Channels of oscilloscope can only measure V relative to ground.

for CH1 & CH2, they are internally connected, ^{so} otherwise short-circuit happens.

Measure $V_R = V - V_z$.

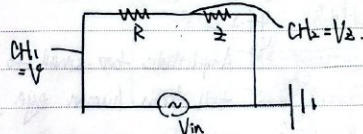

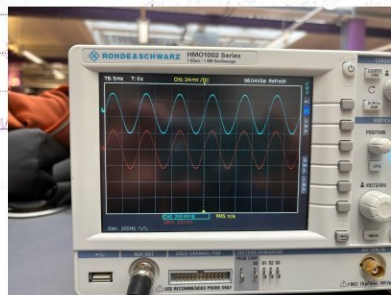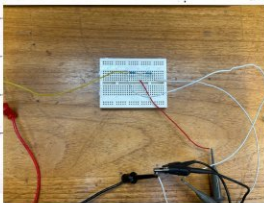when $R = z = 1k\Omega$, $V_R = V_z$ by using "MATH" on CRO:



when $V_R \neq V_z$, $z = R \cdot \frac{V_z}{V_R}$.



We use auto-measure and cursor to test which one is more accurate:

Peak-Peak auto-measure:				
V_z/V_R	V_R/V_R	R/z	$z_{\text{calculated}}$	z_{Actual}
2.60	2.80	1000	929	900
4.32	1.72	1000	2.51k	2.88k
3.92	2.04	1000	1.92k	2.14k
4.88	91.5m	1000	5.31k	4.68k
Cursor measure:				
2.60	3.00	1000	897	
4.27	1.55	1000	2.73k	
3.87	1.80	1000	2.15k	
4.73	700.3m	1000	6.75k	

They give error:

Auto:

Cursor measure

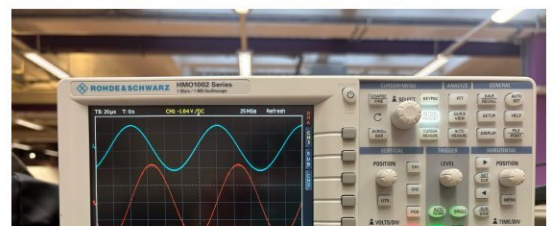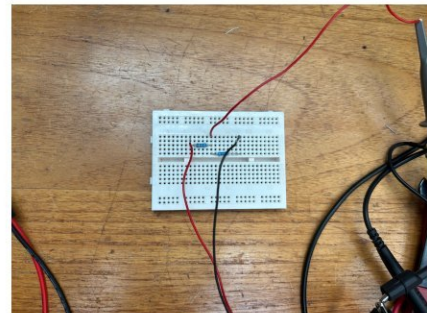

$5.22/10.2$ $5.11/10.2$ $0.533/1.0$ $0.533/1.0$
 12.8% 4.51%
 10.3% 0.467%
 13.5% 44.2%

$\hookrightarrow$ Amplitude too small to tell from human eye.

So in conclusion, $Z = R \frac{V_2}{V_1}$ is true.

Auto-measure has larger error, but still reliable; it's much faster and easier.

Note. In experiment I used varied numbers of resistance because I thought that was uncertainty, and I used the readings on multi-meter. Then I found when I was using multi-meter, I




actually connected myself in parallel with resistor, which is the reason why resistance is not same as written (always smaller). From then on I know, and I use the written value, which proved to be accurate.

Challenge: Measure source impedance of the signal generator.

In this experiment, we only need CH_1 .

Circuit is like:

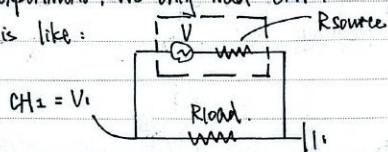

where unknown are R_{source} and V .

$$\therefore V_1 = V \cdot \frac{R_{load}}{R_{load} + R_{source}}$$

$$V_1 / V = R_{load} / R$$

$$4.84 / 4.08 = 0.986k$$

$$4.08 / 4.40 = 0.927k$$

$$4.40 / 4.40 = 1.000k$$

$$\therefore \begin{cases} 4.08 = V \cdot \frac{1.98}{1.98 + R_{source}} \\ 4.40 = V \cdot \frac{8.69}{8.69 + R_{source}} \end{cases} \Rightarrow \begin{cases} R_{source} = 15.9\Omega \\ V = 4.41V \end{cases}$$

check for 3rd part: LHS = 4.84

$$RHS = \frac{9.86}{15.9 + 9.86} \times 4.41 = 4.34$$

$$\therefore \text{Error} = \frac{4.84 - 4.34}{4.84} = 10.3\% \Rightarrow \text{Medium.}$$

which gives 15.9Ω source impedance.

Handwritten signature